

Student name: Xu Miao Date of submission: 5.27

Lab 3. Research on DC drive PWM converters

- Part 1. Evaluate missing parameters

- Source data

$$U_{s_rated}=220;$$

- Source voltage, V;

$$n_{rated}=750;$$

- Nominal rotating speed, rpm;

$$P=170;$$

- Power, W;

$$f_{sw}=5000;$$

- PWM frequency, Hz;

$$R_a=27.2;$$

- Resistance of DC machine winding, Ohm;

$$L_a=0.128;$$

- Armature inductance, H, % $\tau_e=L_a/R_a$;

$$J_s=0.004;$$

- Moment of inertia, kg*m²;

$$K_{eff}=0.9045;$$

- Efficiency, %

Evaluations:

$$I_{a_rated} = \frac{P}{U_{s_rated}} = 0.7727 \quad - \text{Anchor nominal current of DC machine, A;}$$

$$I_{a_sc} = \frac{U_{s_rated}}{R_a} = 8.0882 \quad - \text{Short circuit current, A;}$$

$$\omega_{m_rated} = \frac{2*\pi*n_{rated}}{60} = 78.5398 \quad - \text{Nominal rotating speed, rad/s;}$$

$$T_{e_rated} = \frac{K_{eff}*P}{\omega_{m_rated}} = 1.9577 \quad - \text{Nominal Torque of the DC machine, N*m;}$$

$$T_{e_max} = 3.5 * T_{e_rated} = 6.8520 \quad - \text{Maximum Torque, N*m;}$$

$$I_{lim} = \frac{T_{e_max}}{T_{e_rated}} = 3.5 I_{a_rated} = 2.7045 \quad - \text{Maximum current limit, A;}$$

$$\tau_e = \frac{L_a}{R_a} = 0.0047 \quad - \text{Electromagnetic time constant, s;}$$

$$k_e = \frac{(U_{s_rated} - R_a * I_{a_rated})}{\omega_{m_rated}} = 2.5335 \quad - \text{EMF constant, V*s/rad;}$$


$$k_m = k_e = 2.5335 \quad - \text{Electromechanical constant, N*m/A;}$$

$$T_{e_st} = k_m * I_{a_sc} = 20.4917 \quad - \text{Starting torque, N*m;}$$

$$\omega_0 = \frac{U_{s_rated}}{k_e} = 86.8359 \quad - \text{Idle speed, rad/s;}$$

$$\tau_m = \frac{J_s * \omega_0}{T_{e_st}} = 0.0170 \quad - \text{Electromechanical time constant, s;}$$

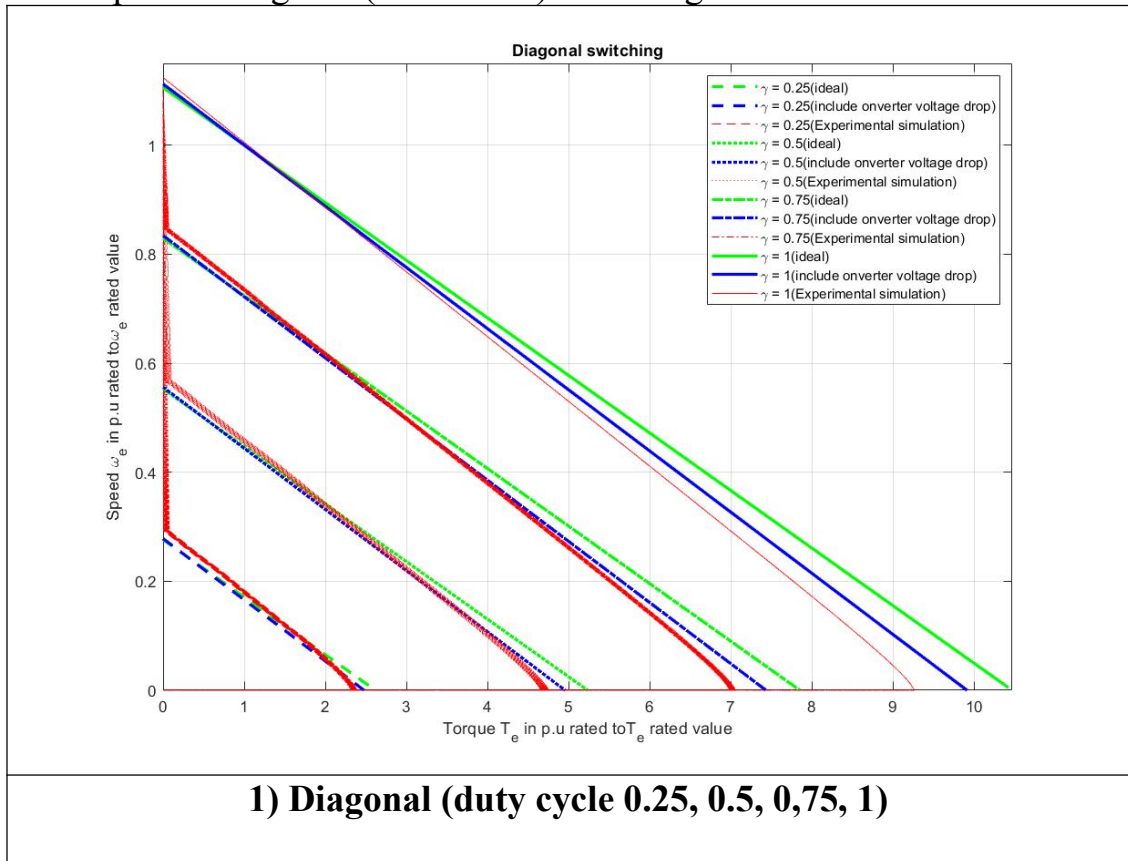- Compare to diagonal (one switch) switching



Conclusion:

From the results of the first part we can get the characteristic curve of the motor **speed ω** , **duty cycle γ** and **torque T_e** of the DC machine, We can draw the following conclusions:

- The Pulse Width Modulator (PWM) provides the motor with an adjustable pulse width with a certain frequency. From the graphs 1) above, we can see the relationship between the **duty cycle γ** and the motor **speed ω** :
 - 1) the larger the pulse width (that is, the **larger** the **duty cycle γ**), the **higher** the motor **speed ω** (because the larger the average voltage supplied to the motor).
 - 2) Conversely, the smaller the pulse width (that is, the **smaller** the **duty cycle γ**), the **lower** the motor **speed ω** (because the average voltage supplied to the motor is smaller).
- Relationship between **torque T_e** of the DC machine and motor **speed ω** :
 - 1) When the **duty cycle γ is constant**, the **torque T_e** and motor **speed ω** have a **linear inverse relationship**

Part 2. Evaluate parameters of the system with PWM

Transistor switched on circuit parameters

% - Forward voltage V_f (V) (For MOSFET may be considered equal to 0)

$$V_{f_vt} = 1.2$$

% - Forward voltage V_f at rated current I_{lim} (V)

$$V_{f_Ia} = 1.3 \quad (\text{replace with})$$

% - FET resistance R_{on} (Ohm)

$$R_{on_vt} = (V_{f_Ia} - V_{f_vt}) / I_{lim}$$

Snubber circuit parameters

% - Snubber resistance R_s (Ohm)

$$C_s = 330e-9$$

% - Snubber capacitance C_s (F)

$$R_s = 1e6$$

Reverse (antiparallel) diode parameters

% - Internal (antiparallel) diode forward voltage V_f (V)

$$V_{f_rd} = 0.65$$

% - Internal (antiparallel) diode forward voltage at rated current I_{lim} (V)

$$V_{f_Ia_rd} = 0.75$$

% - Internal (antiparallel) diode resistance R_d (Ohm)

$$R_{on_rd} = (V_{f_Ia} - V_{f_rd}) / I_{lim}$$

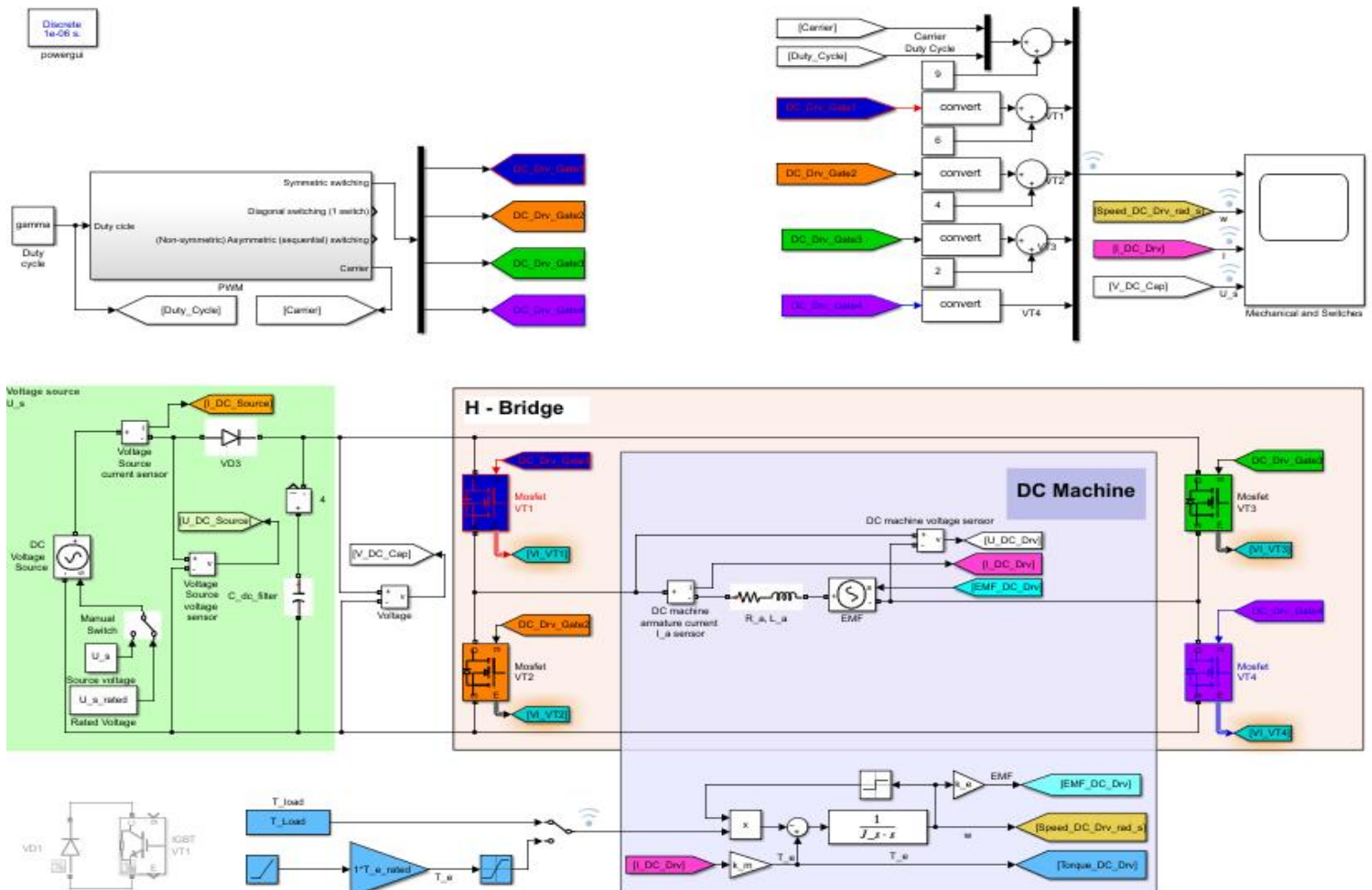


Figure 1 – DC drive system under test

parameter modification

As shown in Figure 1, the transistor used in the model is a Mosfet transistor, and the Forward voltage of this transistor is considered to be equal to 0, so the given parameter is modified as:

Transistor switched on circuit parameters

% - Forward voltage V_f (V) (For MOSFET may be considered equal to 0)

$$V_{f_vt} = 0$$


% - Forward voltage V_f at rated current I_{lim} (V)


$$V_{f_Ia} = 1.3 \text{ (replace with)}$$

% - FET resistance R_{on} (Ohm)


$$R_{on_vt} = (V_{f_Ia} - V_{f_vt}) / I_{lim}$$

Part 3. Simulation results

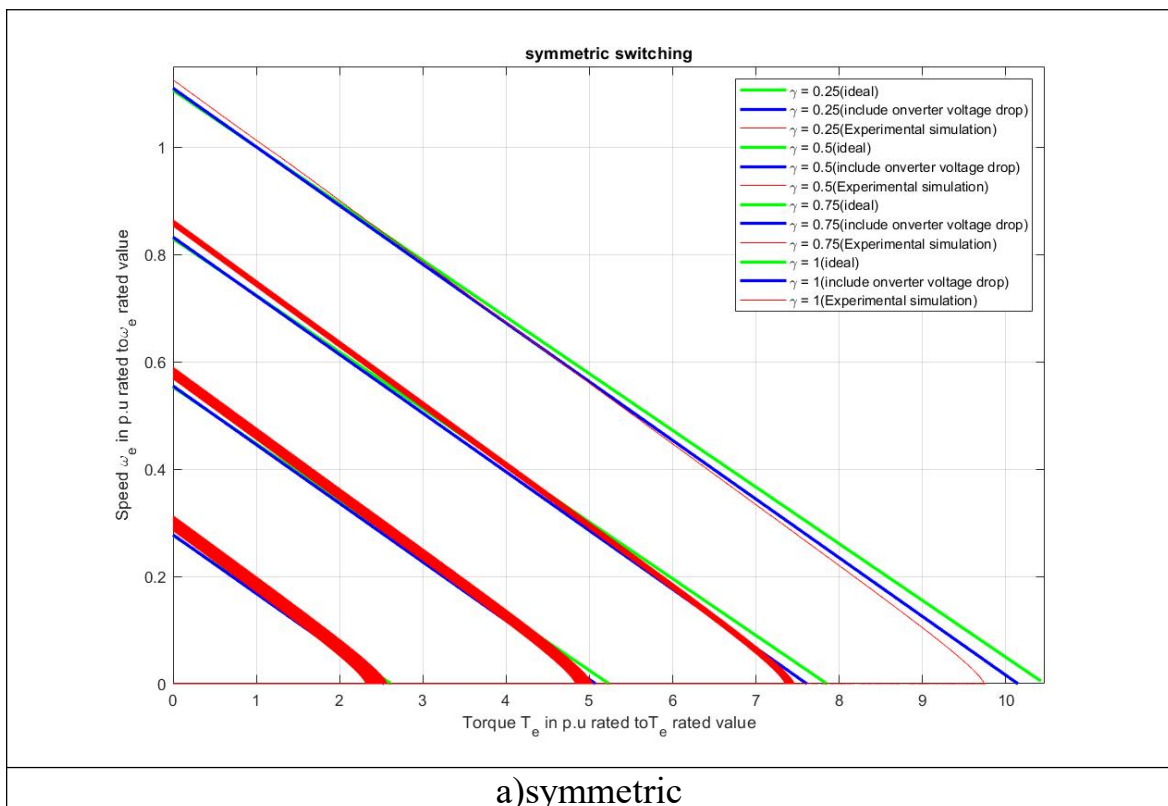

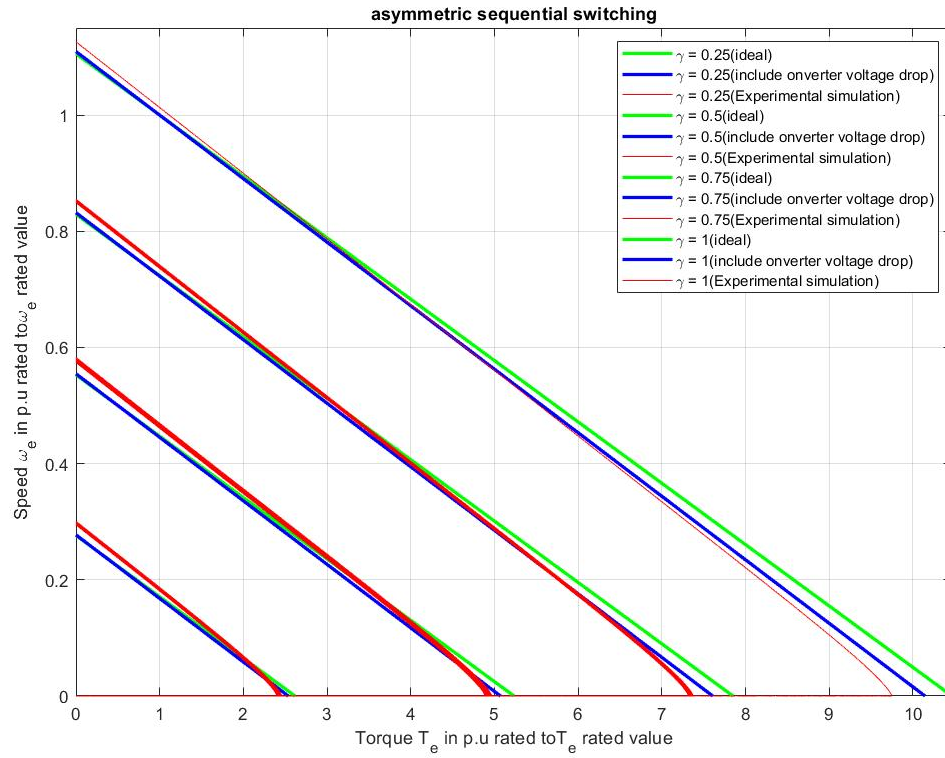

b) asymmetric sequential

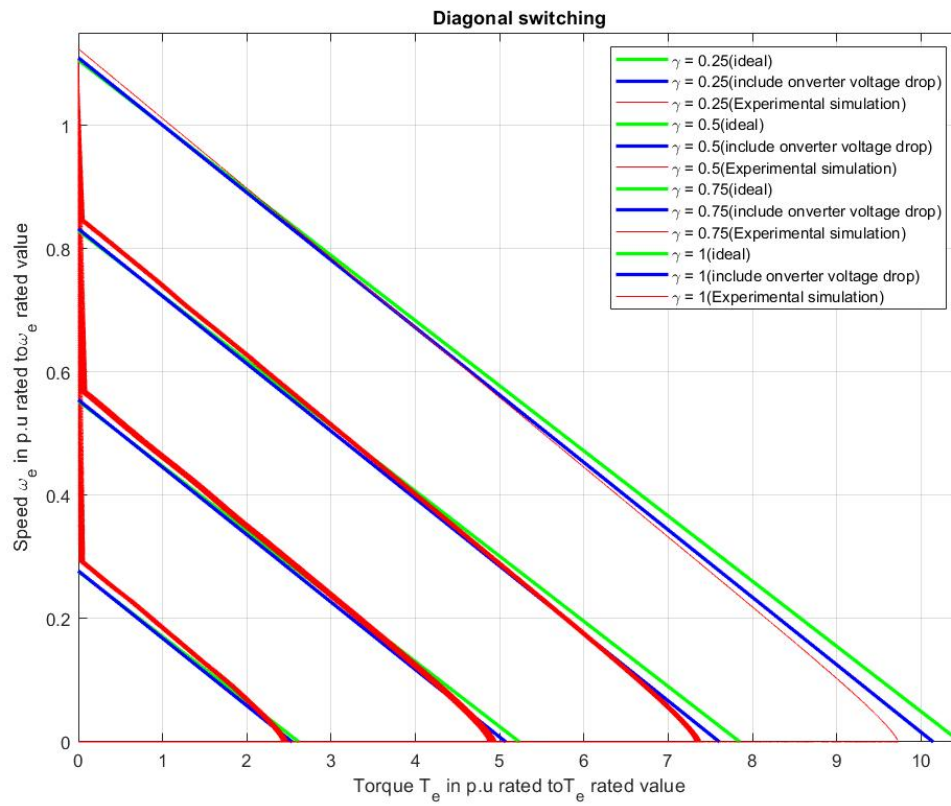

c) Diagonal (duty cycle 0.25, 0.5, 0.75, 1)

Figure 2 – DC drive mechanical characteristics

Conclusion:

- PWM switching methods include:
 - 1) Symmetric
 - 2) Asymmetric
 - 3) Non-symmetric sequential switching
- According to the simulation results in Figures a), b), and c), there are errors between the DC drive simulation results of the PWM converter and the ideal switching and considering the parameters of the converter.
- the energy performance of DC drive with PWM converter is always determined by additional losses in the copper of the machine and switching losses in power transistors

- Analyze drive parameters with different pulse width with duty cycle $\gamma = 0.75$ and $T_{load} = 3.5 * T_{e_rated}$

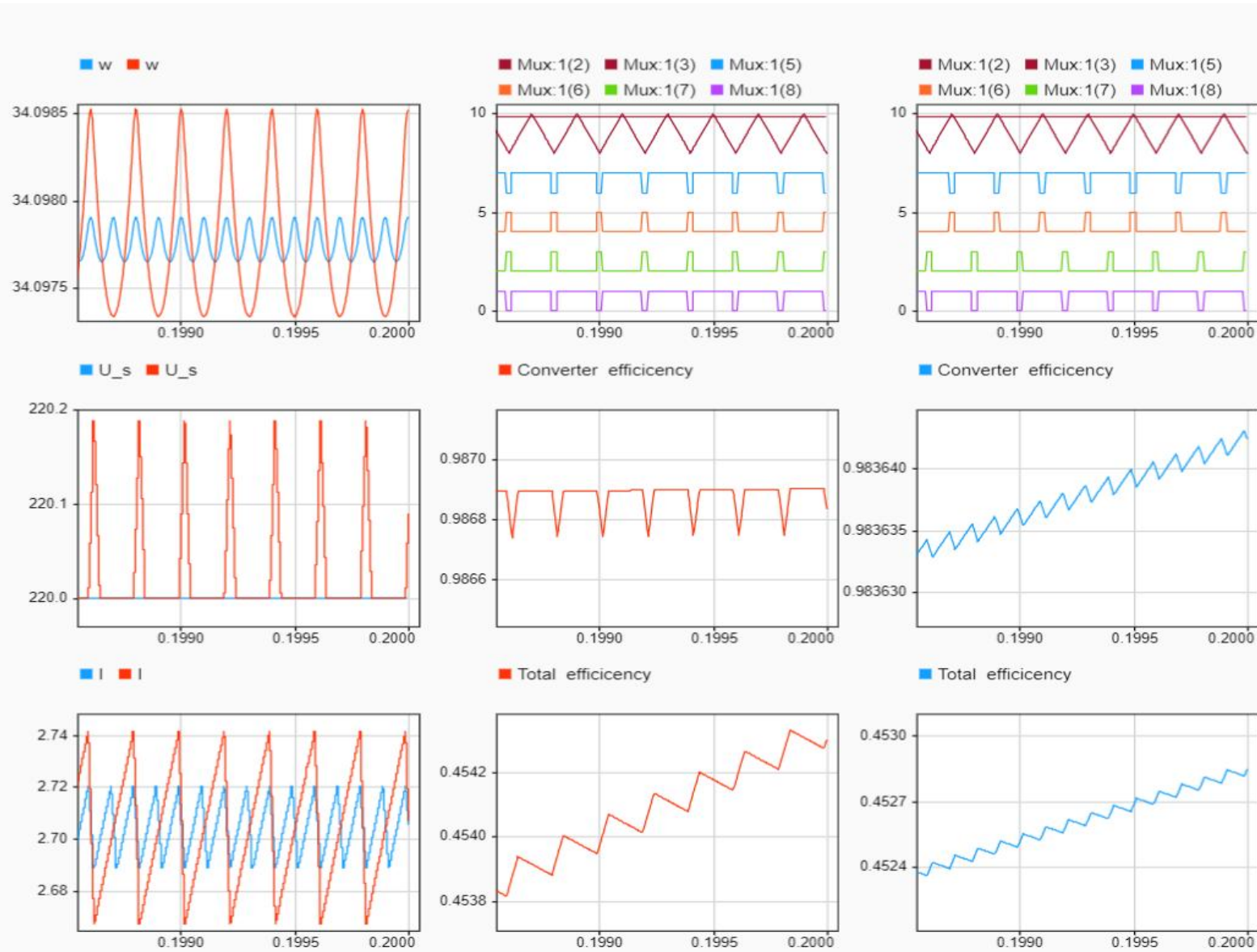


Figure 3 – DC Drive with PWM converter efficiency

The **red line** in the above figure represents **symmetric switching**, and the **blue line** represents **asymmetric switching**

Optimal switching frequency evaluation (**symmetrical switching**)

$$f_{sw_opt} = 0.332 \sqrt[3]{\frac{\alpha_k r_a^2}{L_a^2(t_+ + t_-)}} = 3.9526 \times 10^3 \text{ Hz}$$

Optimal switching frequency evaluation (**asymmetric switching**)

$$f_{sw_opt} = 0.26 \sqrt[3]{\frac{\alpha_k r_a^2}{L_a^2(t_+ + t_-)}} = 3.096 \times 10^3 \text{ Hz}$$

Conclusion:

- When α_k and L_a , R_a , t_+ , t_- are the same, the frequency of **symmetric switching** is higher than the frequency of **asymmetric switching**

- Both average **converter efficiency** and **average total efficiency** are higher for **symmetrical switching** than for **asymmetrical switching**
- **Asymmetric switching** is more **stable** than symmetrical switching (because the **angular velocity ω** , **voltage U_s** , and **current I** of **symmetrical switching** fluctuate more than **asymmetric switching**)